

BAL BHARATI PUBLIC SCHOOL

Ganga Ram Hospital Marg, New Delhi-60

CLASS –XII

ASSIGNMENT- 5

SUBJECT – COMPUTER SCIENCE

TOPIC – Boolean Algebra

1. State Demorgan's laws. Verify one of the laws using truth table.
2. State and prove
 - a. Law of Duality. Give the dual of $(A+BC+(AB)')$.
 - b. Distributive Law
 - c. Idempotent Law
 - d. Absorption Law
3. Reduce the following Boolean expression:
 - a. $H(U,V,W,Z) = \sum(0,1,4,5,6,7,11,12,13,14,15)$
 - b. $F(A,B,C,D) = \pi(5,6,7,8,9,12,13,14,15)$
4. Verify the following algebraically:
 - a. $X.Y'.Z+X.Y'.Z'+X'.Y'.Z = X.Y'+Y'$
 - b. $XY+YZ+Y'Z = XY+Z$
 - c. $XY+YZ+YZ'=Y$
5. Draw a logic circuit diagram for the following Boolean expressions:
 - a. $A.(B+C')$
 - b. $X.Y'+Y.Z'$ (using NAND gates only)
 - c. $(A+B)(A+B')$
 - d. $X(Y'+Z)$ (using NOR gate only)
6. Given the following truth table, derive the SOP and POS

X	Y	Z	G(X,Y,Z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

7. A majority gate is a digital circuit whose output is 1 if the majority of inputs are 1's. The output is 0 otherwise. By means of a truth table, find the Boolean function implemented by 3-input majority gates.

8. Simplify using K-map for:

- a. $F(w,x,y,z) = M_2 + M_3 + M_4 + M_5 + M_6 + M_7 + M_9 + M_{11} + M_{13}$ (M-Maxterm, m-Minterm)
- b. $F(a,b,c,d) = \pi(1,2,4,5,7,10,15)$
- c. $F(w,x,y,z) = m_2 + m_3 + m_5 + m_6 + m_7 + m_9 + m_{11} + m_{13}$ (M-Maxterm, m-Minterm)
- d. $F(a,b,c,d) = \Sigma(0,7,8,9,10)$
- e. $y't' + y'z' + yzt' + yz't'$

9. Use the NAND gate to form

- a. Two input OR gate
- b. Two-input AND gate
- c. NOT gate

10. Use the NOR gate to form

- a. Two input OR gate
- b. Two-input AND gate
- c. NOT gate