

ALTERNATING CURRENT

Test Paper-III

MAX MARKS: 30

TIME: 90Mts

Sl. No.	QUESTION	ANSWER PAGE	MARKS
1	What is purpose of a transformer? Give the principle on which a transformer works.	Page:259	½ + ½
2	Explain the working of a transformer with a neat labelled diagram	Page:260	3
3	Give any two arrangements in which the coils can be placed to form transformer	Page:260	½ + ½
4	Give the differences between step up transformer and step down transformer	Page:261	2
5	What are the different losses in case of a transformer? How will you reduce these losses?	Page:261	3

Marks: 12 marks

Match the following

Page: 262

Part-A

Part-B

- 1 Rms value of current
- 2 Mean value of current over complete cycle
- 3 Ac voltage
- 4 Capacitive reactance
- 5 Inductive reactance
- 6 Power factor
- 7 Q-factor
- 8 Resonant frequency
- 9 Average power loss over a complete cycle

$$I = 0.707 i_m$$

$$V = V_m \sin \omega t$$

$$X_L = \omega L$$

$$\cos \phi$$

$$\omega_0 L/R$$

$$\text{zero}$$

$$\omega_0 = 1/\sqrt{LC}$$

$$VI \cos \phi$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

- 10 Impedance of LCR series circuit
- 11 Voltage across the secondary of a transformer
- 12 Current through the primary of a transformer

$$I_S = \left[\frac{N_p}{N_s} \right] I_p$$

$$X_C = 1/\omega C$$

$$V_S = \left[\frac{N_s}{N_p} \right] V_p$$

Write the dimensional formula of the following

8 marks

Page: 264

- 1 Rms value of current -----
- 2 rms voltage-----
- 3 Capacitive reactance-----
- 4 Inductive reactance-----
- 5 Power factor-----
- 6 Q-factor-----
- 7 Resonant frequency-----
- 8 Impedance of LCR series circuit-----

ZIET BBSR