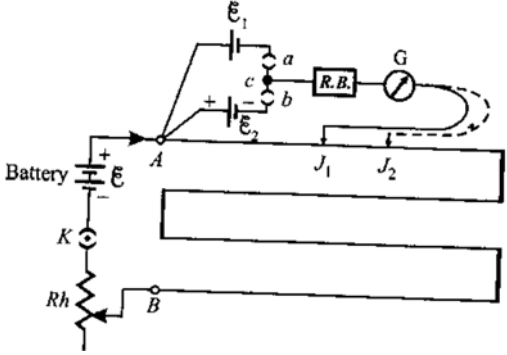
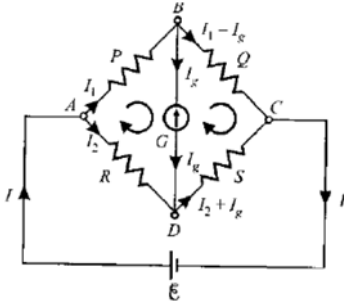
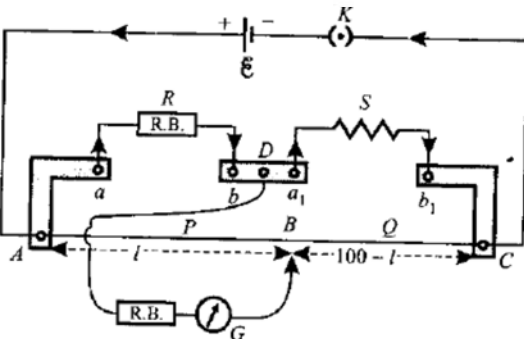



**CLASS XII MLL Questions****Current Electricity**


Q.1	. The sequence of bands marked on a carbon resistor is red, red. Red silver. What is the value of resistance? Ans:- $22 \times 10^2 \pm 10\%$	1
Q.2	Does the drift velocity vary with the magnitude of the current through the conductor? Explain.  Ans. Yes. Drift velocity, $V_d = \frac{I}{ned}$ . i.e. $V_d \propto I$	2
Q.3	. A wire is cut into half. What is the effect on its specific resistance? Ans :- No effect.	1
Q.4	:- Why do we prefer a potentiometer with a longer bridge wire? Ans:- When the bridge wire is longer the potential gradient is smaller. Smaller the potential gradient more is the sensitivity of potentiometer wire.	1
Q.5	What are the factors affecting internal resistance of a cell Ans-Nature of electrolyte  Separation between the electrode	2
Q.6	Establish a relation between the current and drift velocity Ans-Page 97 NCERT	2
Q.7	Describe with the help of circuit diagram how a potentiometer can be used to compare the e.m.f. of two cells. Ans-Potential gradient – The potential drop per unit of length of the potentiometer.  Method to compare emf of two cells –  $\xi_1 = kl$ when a is closed	3

	 <p> <math>\xi_2 = kl_2</math> when b is closed  <math>\therefore \xi_1 = kl_1</math>  <math>\xi_2 = kl_1</math>  <math>\xi_3 = \xi_1 \frac{l_2}{l}</math> </p> <p>Causes for one sided deflection of potentiometer</p> <ul style="list-style-type: none"> <li>(i) +ve terminals of all cells are not connected at one point.</li> <li>(ii) emf of driving cell is less than emf of cell.</li> </ul>	
Q.8	<p>Define resistivity and state its SI unit. State and explain how the resistivity of a conductor varies with temperature</p> <p>Ans-Resistivity is the resistance of a conductor of that material having unit length and unit area of cross-section.</p> <p>S.I. unit = ohm metre (<math>\Omega M</math>)</p> $\text{Resistivity} = \frac{M}{ne^2 \uparrow} \uparrow$ <p>With increase in temperature, the electrons suffer collisions more frequently and the relaxation time <math>\tau</math> decreases. Hence, the resistivity of a conductor increases.</p>	3
Q.9	<p>(a) Three resistors <math>1 \Omega</math>, <math>2 \Omega</math>, and <math>3 \Omega</math> are combined in series. What is the total resistance of the combination? (b) If the combination is connected to a battery of emf <math>12 \text{ V}</math> and negligible internal resistance, obtain the potential drop across each resistor</p> <p>Ans-</p> <p>(a) Three resistors of resistances <math>1 \Omega</math>, <math>2 \Omega</math>, and <math>3 \Omega</math> are combined in series. Total resistance of</p>	3

	<p>the combination is given by the algebraic sum of individual resistances.</p> <p>Total resistance = <math>1 + 2 + 3 = 6 \Omega</math></p> <p>(b) Current flowing through the circuit = <math>I</math></p> <p>Emf of the battery, <math>E = 12 \text{ V}</math></p> <p>Total resistance of the circuit, <math>R = 6 \Omega</math></p> <p>The relation for current using Ohm's law is,</p> $I = \frac{E}{R}$ $= \frac{12}{6} = 2 \text{ A}$ <p>Potential drop across <math>1 \Omega</math> resistor = <math>V_1</math></p> <p>From Ohm's law, the value of <math>V_1</math> can be obtained as</p> $V_1 = 2 \times 1 = 2 \text{ V} \dots \text{(i)}$ <p>Potential drop across <math>2 \Omega</math> resistor = <math>V_2</math></p> <p>Again, from Ohm's law, the value of <math>V_2</math> can be obtained as</p> $V_2 = 2 \times 2 = 4 \text{ V} \dots \text{(ii)}$ <p>Potential drop across <math>3 \Omega</math> resistor = <math>V_3</math></p> <p>Again, from Ohm's law, the value of <math>V_3</math> can be obtained as</p> $V_3 = 2 \times 3 = 6 \text{ V} \dots \text{(iii)}$ <p>Therefore, the potential drop across <math>1 \Omega</math>, <math>2 \Omega</math>, and <math>3 \Omega</math> resistors are <math>2 \text{ V}</math>, <math>4 \text{ V}</math>, and <math>6 \text{ V}</math> respectively.</p>	
Q.10	<p>Derive the balance condition of Wheat Stone bridge .also draw the circuit diagram to find the specific rsistance by meter bridge.</p> <p>Ans-</p> 	3

	<p>Kirchoff's first law – In an electrical circuit, the sum of input current is equal to output current.</p> <p>Second Law - <math>\sum \xi = \sum IR</math></p> <p>Applying kirchoff's law in</p> <p>100P ABDA,</p> $I_1 P + I_g G - I_2 R = 0$ <p>In 100p BCDB,</p> $(I_1 - I_g) - (I_2 + I_g)S - GI_g = 0$ <p>In balanced condition, <math>I_g = 0</math></p> $I_1 P - I_2 R = 0$ $I_1 \theta - I_2 S = 0$ $\frac{P}{Q} = \frac{R}{S}$ <p>circuit diag. to determine the unknown resistance.</p> 	
Q.11	<p>What do you mean by relaxation time of free electrons in metals?</p> <p>Ans-It is average time between two successive collisions between electrons in conductor or semiconductor</p>	1
Q.12	<p>Will the drift speed of free electrons in a metallic conductor increases or decreases with increase or decrease in temperature?</p>	2

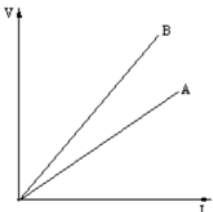	Ans-With increase in temperature, resistance increase and hence drift velocity decreases.	
Q.13	<p>V – I graphs for parallel and series combination of two metallic resistors are shown in figure. Which graph represents parallel combination? Justify your answer-.</p> 	2
Q.14	<p>Describe the formula for the equivalent EMF and internal resistance for the parallel combination of two cells with EMF <math>E_1</math> and <math>E_2</math> and internal resistances <math>r_1</math> and <math>r_2</math> respectively. What is the corresponding formula for the series combination?</p> <p>Ans-Derivation for parallel combination</p> $E = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$ $r = \frac{r_1 r_2}{r_1 + r_2}$ <p>(ii) Series combination formula  <math>(E = E_1 + E_2), (r = r_1 + r_2)</math></p> <p>(iii) Numerical</p> $\left[ \frac{2+1}{1+2+R} = \frac{(1 \times 1 + 2 \times 2)/(1+2)}{\frac{1 \times 2}{1+2}} \Rightarrow R = \frac{9}{4} \Omega ; \text{More in series} \right]$	3
Q.15	<p>Why the resistance of the conductor increases with rise in temperature?</p> <p>Ans:- resistance <math>R = \frac{m l}{n A e^2 C}</math>.</p> <p>When the temperature of conductor is increased the electron begin to collide more frequently with atoms and ions, so the relaxation time is decreased consequently the resistance increases.</p>	2
Q.16	<p>A carbon resistor of <math>47 \times 10^3 \pm 5\%</math> is to be marked with rings of different colours for its identification write the sequence of colours?</p> <p>Ans:- Yellow, Violet, Orange , Gold.</p>	1
Q.17	<p>State the Kirchoff's laws</p> <p>Ans – First law- Junction Rule or Current Law          In an electric circuit, the algebraic sum of currents at any junction is zero</p> <p>Second Law- Loop Rule or Potential Law          The algebraic sum of the emfs of any loop of a circuit is equal to the sum of the product of the</p>	2

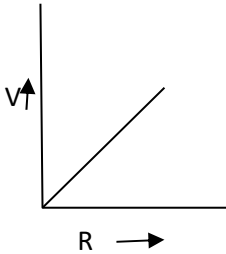	currents and resistances in it.	
Q.18	<p>Two wires of equal length, one of copper and other of manganin have same resistance .Which is thicker?</p> <p>Ans-<math>R_{\text{copper}} = R_{\text{manganin}}</math></p> <p>We know that <math>R = \frac{\rho l}{A}</math></p> <p>For same length, <math>\frac{\rho_c}{A_c} = \frac{\rho_m}{A_m}</math></p> <p><math>\rho_c &lt; \rho_m</math></p> <p>So, <math>A_c &lt; A_m</math></p> <p>Therefore manganin is thicker than copper.</p>	3
Q.19	<p>If the current supplied to a variable resistor, is constant. Draw a graph between Voltage and Resistance.</p> 	1
Q.20	<p>Name the material used for making standard resistance. Give reason of choice.</p> <p>Ans –Manganin ,constantan or Nichrome.</p> <p>High resistivity and low temperature coefficient of resistance</p>	2