
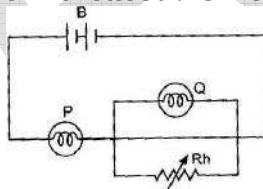


**REVISION ASSIGNMENT**  
**PHYSICS (CLASS XII)**  
**UNIT 2 - CURRENT ELECTRICITY**

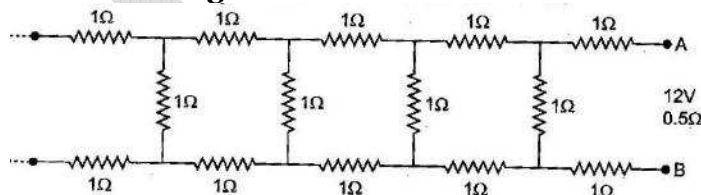1. The electron drift speed in a metallic conductor is only a few  $\text{mm s}^{-1}$  for currents in the range of the few amperes. How then is the current established almost at the instant the circuit is closed?
2. When electrons drift in a metal from lower to higher potential, does it mean that the free electrons of the metal are moving in the same direction?
3. Two conducting wires X and Y of same diameter but different materials are joined in series across a battery. If the number density of electrons in X is twice that in Y, find the ratio of drift velocity of electrons in the two wires.
4. Two wires one of manganin and the other of copper have equal length and equal resistance. Which one of these wires will be thicker?
5. Two 120 V light bulbs, one of 25 W and the other of 200 W were connected in series across a 240 V line. One bulb burnt out almost instantaneously. Which one was burnt and why?
6. A cell of emf  $E$  and internal resistance  $r$  is connected across an external resistance  $R$ . Plot a graph showing the variation of P.D. across  $R$ , versus  $R$ .
7. Draw the graphs showing the variation of resistivity with temperature for (i) nichrome and (ii) silicon.
8. The circuit shown in the diagram contains a battery 'B', a rheostat ' $R_h$ ' and identical lamps P and Q. What will happen to the brightness of the lamps, if the resistance through the rheostat is increased? Give reasons.



9. Determine the current drawn from a 12 V supply with internal resistance  $0.5 \Omega$  by the infinite network shown in fig. Each resistor has  $1 \Omega$  resistance.



10. In a meter bridge, the null point is found at a distance of 40 cm from A. If a resistance of  $12 \Omega$  is connected in parallel with S, the null point occurs at 50.0 cm from A. Determine the values of R and S.

