

# SEMICONDUCTOR DEVICES

## Test Paper-II

**MAX MARKS: 30**

**TIME: 90Mts**

Sl. No.	QUESTION	ANSWER PAGE	MARKS
1	What is a semiconductor diode? Give the symbol representing the same.	Page:478	1
2	Discuss about the forward bias condition of a p-n junction diode. Also draw its characteristic curve.	Page:479	3
3	Discuss about the reverse bias condition of a p-n junction diode. Also draw its characteristic curve.	Page:480	3
4	Explain the working of a semiconductor diode as a Half- wave rectifier. Give the input and output waveforms.	Page:483	3
5	Explain the working of a diode as a Full wave rectifier and give its input output waveforms.	Page:484	3
6	What is a zener Diode? Explain the working of a zener diode as a voltage regulator.	Page:485	3
7	In a zener regulated power supply a zener diode with $V_z=6.0V$ is used for regulation. The load current is to be $4.0mA$ and the unregulated input is $10.0V$ . What should be the value of series resistors?	Page:486	3
8	What is a photodiode? Explain the working of it.	Page:487	3
9	The current in the forward bias (mA) is known to be more than the current in the reverse bias ( $\mu A$ ). What is the reason then to operate the photodiode in reverse bias?	Page:487	3
10	What is an LED? Briefly explain the working of it. What are its advantages over incandescent low power lamps?	Page:488	3
11	Match the following	Page:486 to 489	
	Group-A	Group-B	
	1. LED	a. When illuminated with light electron –hole Pairs are generated	2
	2. Photodiode	b. convert electrical energy into light	
	3. Solar cell	c. voltage regulator	
	4. Zener diode	d. generates emf when light falls on it.	